

22. VHDL CODE FOR 1-BIT COMPARATOR (STRUCTURAL):

```
library IEEE;
```

```
use IEEE.STD_LOGIC_1164.ALL; use IEEE.STD_LOGIC_ARITH.ALL;
```

```
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

```
entity comp is
```

```
  Port (
```

```
    a, b : in STD_LOGIC;
```

```
    y : out STD_LOGIC_VECTOR (2 downto 0)
```

```
  );
```

```
end comp;
```

```
architecture struct of comp is
```

```
  -- Component Declarations
```

```
  component and1
```

```
    port(l, m : in std_logic; n : out std_logic);
```

```
  end component;
```

```
  component xnor1
```

```
    port(p, q : in std_logic; r : out std_logic);
```


```
  end component;
```

```
  component notgate1
```

```
    port(s : in std_logic; t : out std_logic);
```

```
  end component;
```

```
  -- Internal Signals
```

 

A	B	Y1 (A>B)	Y2 (A = B)	Y3 (A < B)
0	0	0	1	0
0	1	0	0	1
1	0	1	0	0
1	1	0	1	0

```
signal s1, s2 : std_logic;
```

```
begin
```

```
-- Logic for comparator output
```

```
u1 : and1 port map(a, s2, y(0)); -- a > b
```

```
u2 : and1 port map(s1, b, y(1)); -- a < b
```

```
u3 : xnor1 port map(a, b, y(2)); -- a = b
```

```
u4 : notgate1 port map(a, s1);
```

```
u5 : notgate1 port map(b, s2);
```

```
end struct;
```

