

22. VHDL CODE FOR DECODER 3:8 (STRUCTURAL):


```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_ARITH.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity dec is
    Port (    a, b : in  STD_LOGIC;
            y  : out STD_LOGIC_VECTOR (3 downto 0)
    );
end dec;

architecture Behavioral of dec is

```

 

-- Components, entity and architecture must be declared separately

component and1 is

```
    port(p, q : in std_logic; r : out std_logic);
```

end component;

component not1 is

```
    port(d : in std_logic; e : out std_logic);
```

end component;

```
signal s1, s2 : std_logic;
```

begin

```
u1: and1 port map(s1, s2, y(0));
```

```
u2: and1 port map(s1, b, y(1));
```

```
u3: and1 port map(a, s2,  y(2));
```

```
u4: and1 port map(a, b,  y(3));
```

```
u5: not1 port map(a, s1);
```

```
u6: not1 port map(b, s2);
```

end Behavioral;

